
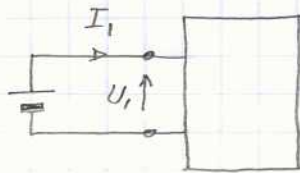


Opg. nr. 1

$$U_1 = 45,5 \text{ V}$$

$$I_1 = 1,75 \text{ A}$$

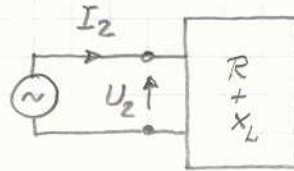

$$U_2 = 230 \text{ V}$$

$$f = 50 \text{ Hz}$$

$$I_2 = 7,65 \text{ A}$$

$$a) \quad R = \frac{U_1}{I_1} = \frac{45,5}{1,75} = 26,00 \approx \underline{\underline{26,0 \Omega}}$$

$$b) \quad Z = \frac{U_2}{I_2} = \frac{230}{7,65} = 30,07 \Omega$$

$$X_L = \sqrt{Z^2 - R^2} = \sqrt{30,07^2 - 26,00^2} = 15,11 \Omega$$

$$X_L = 2\pi fL$$

$$L = \frac{X_L}{2\pi f} = \frac{15,11}{2 \cdot \pi \cdot 50} = 0,0481 \approx \underline{\underline{0,048 \text{ H}}}$$

$$c) \quad P_1 = I_1^2 \cdot R = 1,75^2 \cdot 26,0 = 79,63 \approx \underline{\underline{79,6 \text{ W}}}$$


$$d) \quad P_2 = I_2^2 \cdot R = 7,65^2 \cdot 26,0 = 1521,6 \approx \underline{\underline{1522 \text{ W}}}$$

$$e) \quad P_2 = U_2 \cdot I_2 \cdot \cos \varphi$$

$$\cos \varphi = \frac{P_2}{U_2 \cdot I_2} = \frac{1521,6}{230 \cdot 7,65} = 0,8648 \approx \underline{\underline{0,865}}$$

Opg. nr. 2

a)

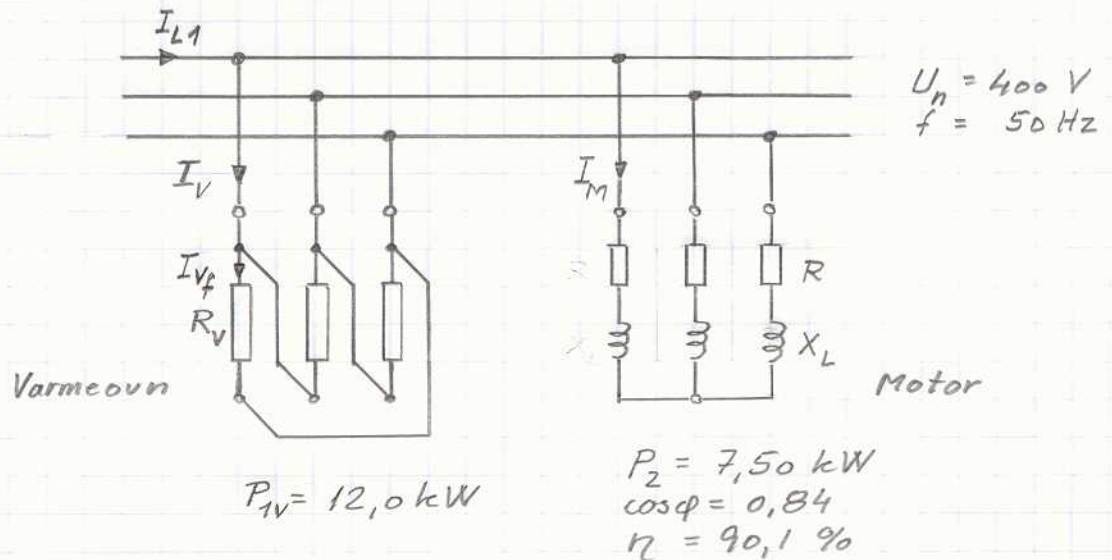

b)

$$P_{1V} = \sqrt{3} \cdot U_n \cdot I_V$$

$$I_V = \frac{P_{1V}}{\sqrt{3} \cdot U_n} = \frac{12000}{\sqrt{3} \cdot 400} = 17,321 \approx \underline{\underline{17,3 \text{ A}}}$$

c)

$$P_{1V} = 3 \cdot I_{Vf}^2 \cdot R_V = 3 \cdot \left(\frac{I_V}{\sqrt{3}}\right)^2 \cdot R_V = I_V^2 \cdot R_V$$

$$R_V = \frac{P_{1V}}{I_V^2} = \frac{12000}{17,321^2} = 40,00 \approx \underline{\underline{40,0 \Omega}}$$

d)

$$\eta = \frac{P_2}{P_{1M}}$$

$$P_{1M} = \frac{P_2}{\eta} = \frac{7500}{0,901} = 8324 \approx \underline{\underline{8,32 \text{ kW}}}$$

e)

$$P_{1M} = \sqrt{3} \cdot U_n \cdot I_M \cdot \cos \phi$$

$$I_M = \frac{P_{1M}}{\sqrt{3} \cdot U_n \cdot \cos \phi} = \frac{8324}{\sqrt{3} \cdot 400 \cdot 0,84} = 14,30 \approx \underline{\underline{14,3 \text{ A}}}$$

f)

$$P_1 = P_{1V} + P_{1M} = 12000 + 8324 = 20324 \approx \underline{\underline{20,3 \text{ kW}}}$$

g)

$$\left. \begin{array}{l} P_{1M} = S_M \cdot \cos \phi \\ Q_M = S_M \cdot \sin \phi \end{array} \right\} \frac{Q}{P} = \tan \phi; \quad Q = Q_V + Q_M = 0 + Q_M$$

$$Q = Q_M = P_{1M} \cdot \tan \phi = 8324 \cdot \tan(\cos^{-1} 0,84) = 5377 \approx \underline{\underline{5,38 \text{ kVAR}}}$$

h)

$$S = \sqrt{P^2 + Q^2} = \sqrt{20324^2 + 5377^2} = 21023 \approx \underline{\underline{21,0 \text{ kVA}}}$$

i)

$$I_{L1} = \frac{S}{\sqrt{3} \cdot U_n} = \frac{21023}{\sqrt{3} \cdot 400} = 30,34 \approx \underline{\underline{30,3 \text{ A}}}$$

Eksamen, 28. maj 2003

Opg. nr. 34-polet asynkronmotor ($p = 2$)Mærkedata: $U_n = 400 \text{ V}$

$$f = 50 \text{ Hz}$$

$$P_2 = 75 \text{ kW}$$

$$I_n = 140 \text{ A}$$

$$\cos \varphi = 0,85$$

$$n_2 = 1485 \text{ min}^{-1}$$

a)
$$n_1 = \frac{f}{p} \cdot 60 = \frac{50}{2} \cdot 60 = 1500 \text{ min}^{-1}$$

$$n_s = n_1 - n_2 = 1500 - 1485 = 15 \text{ min}^{-1}$$

$$s = \frac{n_s}{n_1} \cdot 100\% = \frac{15}{1500} \cdot 100\% = \underline{\underline{1,00\%}}$$

b)
$$P_1 = \sqrt{3} \cdot U_n \cdot I_n \cdot \cos \varphi = \sqrt{3} \cdot 400 \cdot 140 \cdot 0,85 = 82446 \text{ W} \approx \underline{\underline{82,4 \text{ kW}}}$$

c)
$$\eta = \frac{P_2}{P_1} = \frac{75000}{82446} = 0,9097 \approx \underline{\underline{91,0\%}}$$

d)
$$P_2 = M \cdot \omega = M \cdot 2\pi \frac{n_2}{60}$$

$$M = \frac{P_2 \cdot 60}{2\pi \cdot n_2} = \frac{75000 \cdot 60}{2\pi \cdot 1485} = 482,29 \approx \underline{\underline{482 \text{ Nm}}}$$