

$$1) P = 60 \text{ W}, U = 230 \text{ V}$$

$$I = \frac{P}{U} = \frac{60}{230} = \underline{\underline{0,263 \text{ A}}}$$

$$2) L = 200 \text{ m}, A = 1,5 \text{ mm}^2, \rho_{\text{Cu}} = 0,0175 \frac{\Omega \text{ mm}^2}{\text{m}}$$

$$R = \rho_{\text{Cu}} \frac{L}{A} = 0,0175 \cdot \frac{200}{1,5} = \underline{\underline{2,33 \Omega}}$$

$$3) d = 30 \text{ mm}, L = 1000 \text{ m}, \rho_{\text{Al}} = 0,029 \frac{\Omega \text{ mm}^2}{\text{m}}$$

$$A = \frac{\pi}{4} d^2 = \frac{\pi}{4} \cdot 30^2 = 707 \text{ mm}^2$$

$$R = \rho_{\text{Al}} \frac{L}{A} = 0,029 \cdot \frac{1000}{707} = \underline{\underline{0,041 \Omega}}$$

$$J = 10 \frac{\text{A}}{\text{mm}^2} \Rightarrow I = J \cdot A = 10 \cdot 707 = 7070 \text{ A}$$

$$\Delta U = R \cdot I = 0,041 \cdot 7070 = \underline{\underline{290 \text{ V}}}$$

$$4) L = 10 \text{ m}, A = 0,75 \text{ mm}^2, I = 12 \text{ A}, \text{Cu-tråd}$$

$$R = \rho_{\text{Cu}} \frac{L}{A} = 0,0175 \frac{10}{0,75} = 0,233 \Omega$$

$$U = I \cdot R = 12 \cdot 0,233 = \underline{\underline{2,8 \text{ V}}}$$

$$P = I^2 \cdot R = 12^2 \cdot 0,233 = \underline{\underline{33,6 \text{ W}}}$$

$$5) R_1 = 4,75 \Omega, T_1 = 20^\circ\text{C}, R_2 = 6,98 \Omega$$

$$R_2 = R_1 (1 + \alpha(T_2 - T_1)), \quad \alpha_1 = 4 \cdot 10^{-3} \text{ } ^\circ\text{C}^{-1}$$

$$R_2 = R_1 (1 + \alpha(T_2 - T_1))$$

$$\frac{R_2}{R_1} = 1 + \alpha(T_2 - T_1)$$

$$T_2 - T_1 = \frac{1}{\alpha} \left(\frac{R_2}{R_1} - 1 \right)$$

$$T_2 = T_1 + \frac{1}{\alpha} \left(\frac{R_2}{R_1} - 1 \right)$$

$$= 20 + \frac{1}{4 \cdot 10^{-3}} \left(\frac{6,98}{4,75} - 1 \right)$$

$$= 20 + 117 = \underline{\underline{137^\circ\text{C}}}$$

$$6) E = 12,4 \text{ V}, I = 9,5 \text{ A}, U_{kl} = 11,9 \text{ V}$$

$$U_{kl} = E - I \cdot R_i$$

$$R_i = \frac{E - U_{kl}}{I} = \frac{12,4 - 11,9}{9,5} = \underline{\underline{0,053 \Omega}}$$